

---

---

# Verilog Tutorial

---

---

# Outline


- Digital logic (Digital Systems Design and Laboratory)
- Verilog introduction

# Digital logic

- What is digital logic?
- Boolean algebra
- Logic gates
- Combinational logic
- Sequential logic

# What is digital?

Analog

 

Digital



Credit:

[https://commons.wikimedia.org/wiki/File:Analog\\_clock\\_animation.gif](https://commons.wikimedia.org/wiki/File:Analog_clock_animation.gif)

<https://commons.wikimedia.org/wiki/File:Digital.gif>

# What is digital?

Analog view:  
Voltage



Credit:

<https://learn.sparkfun.com/tutorials/how-to-use-an-oscilloscope/using-an-oscilloscope>

# What is digital?

Analog view:  
Voltage



Digital view:  
high (1) / low (0)

Threshold

Credit:

<https://learn.sparkfun.com/tutorials/how-to-use-an-oscilloscope/using-an-oscilloscope>


# Digital logic in computer architecture




Credit:

<https://www.megaprocessor.com/index.html>

# Digital logic in computer architecture

 

PCB board

 

Logic Gate



$$S = A \text{ xor } B$$
$$C = A \text{ and } B$$

Boolean Algebra

Credit:

[https://zh.wikipedia.org/zh-hk/File:Half\\_Adder.svg](https://zh.wikipedia.org/zh-hk/File:Half_Adder.svg)

<https://www.megaprocessor.com/index.html>



# Boolean Algebra

- Variables: Either 0 or 1
- Operators: AND (\*), OR (+), XOR (^) ...

$$S = A \text{ xor } B$$

$$C = A \text{ and } B$$

# Truth table

A way to list all possible input and corresponding output

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

A	B	$A * B$
0	0	0
0	1	0
1	0	0
1	1	1

# Karnaugh-map

- A way to turn truth table into simplified boolean algebra expressions
- For more details: <https://www.youtube.com/watch?v=RO5alU6PpSU>

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

1. Write out our functional spec as a truth table

2. Write down a Boolean expression with terms covering each '1' in the output:

$$Y = \bar{C}\bar{B}A + \bar{C}BA + C\bar{B}\bar{A} + CBA$$

 

3. We'll show how to build a circuit using this equation in the next two slides.

Using K-map:  $Y = AC' + BC$


# Logic gates

- Physical implementation of operations of boolean algebra
- Logic gate examples:
  - Semiconductor: <https://www.youtube.com/watch?v=sTu3LwpF6XI>
  - Water: <https://www.youtube.com/watch?v=lxXaizglscw&t=157s>


AND



OR

 


XOR

 

# Combinational and Sequential Logic

- Combinational
  - output only depends on input
- Sequential
  - output depends on input and memory state
  - seems as combinational logic + register

# Combinational Logic

 

1-bit adder example:


$S = A \text{ xor } B$

$C = A \text{ and } B$

A	B	S
0	0	0
0	1	1
1	0	1
1	1	0

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

# Combinational Logic

 

Seen as functions


$$S = f(A, B)$$

$$C = g(A, B)$$

A	B	S
0	0	0
0	1	1
1	0	1
1	1	0

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


# Sequential Logic

 



 
# Register

- Components that saves state
- Triggered by another signal (clock mostly)




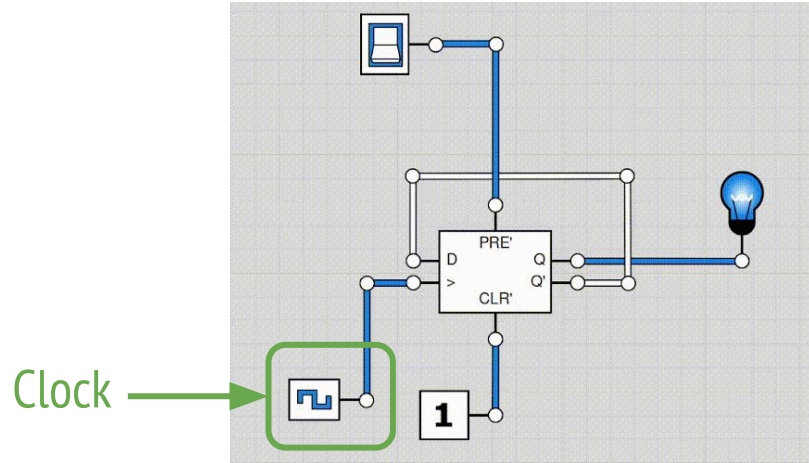
# Register

- Components that save state
- Triggered by another signal (clock mostly)



# Sequential Logic

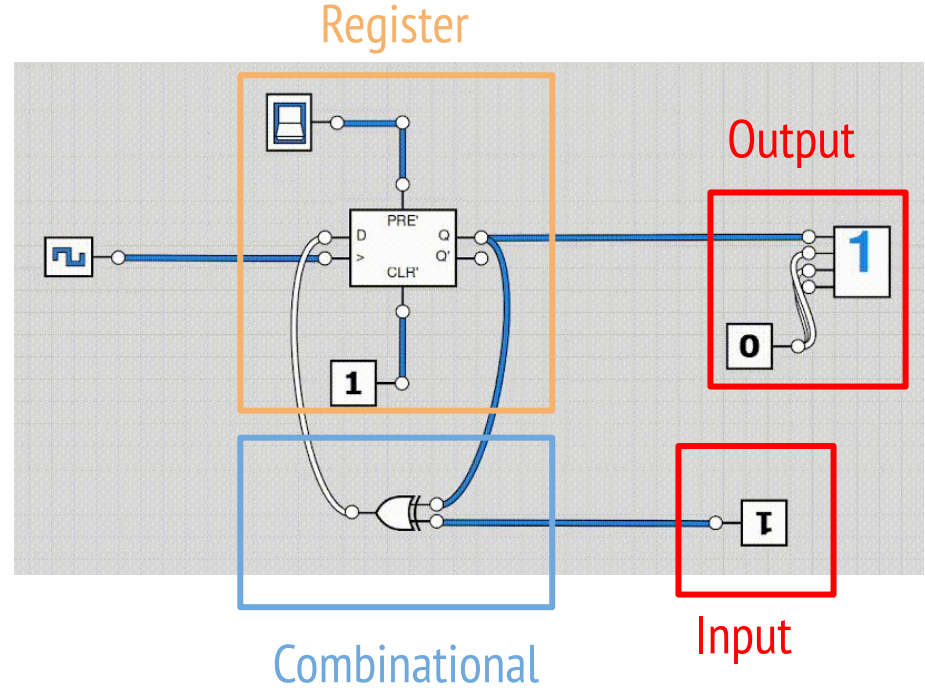 

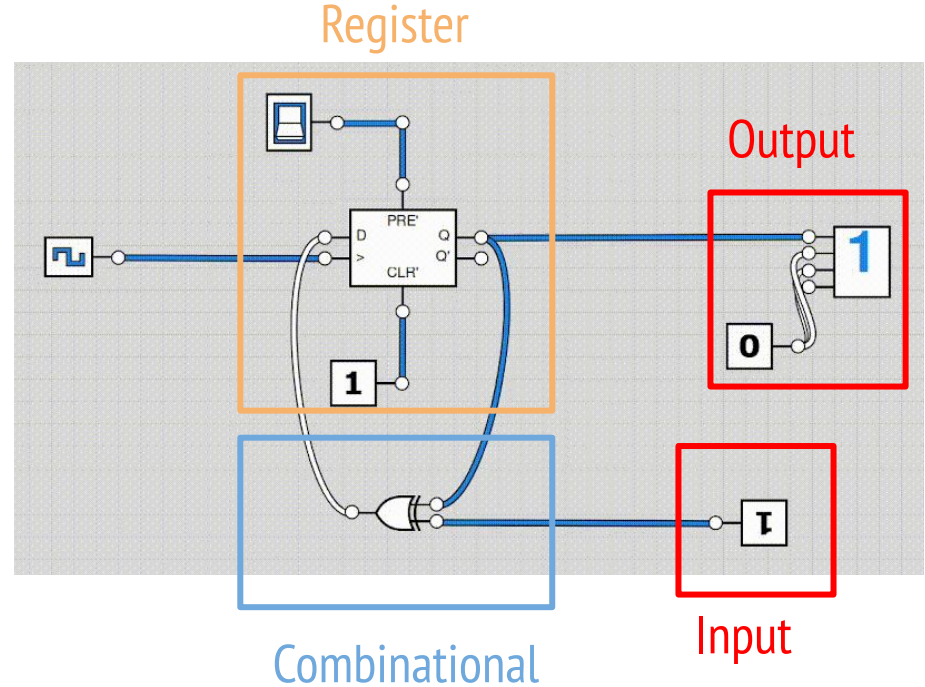
# Wave

- X-axis: time
- Y-axis: logic (0 or 1)



Use clock edge to trigger.  
(posedge 0 to 1, negedge 1 to 0)



# Verilog

- Introduction
- Combinational logic
- Sequential logic
- Testbench

---

# Combinational logic

# Let's build a 1-bit adder

- Operators
- Wire
- Module
- Data

# Operators

- Basically a logic gate
- More details:

<https://class.ece.uw.edu/cadta/verilog/operators.html>


&	bit-wise AND
^ ^ ~ or ~ ^	bit-wise XOR bit-wise XNOR
	bit-wise OR
&&	logical AND
	logical OR



# Assign

- Wire signals together
- Apply logic operations


```
assign s = a & b;
```

 

# Input / Output / Wire

```
3 input a, b;
4 input cin;
5
6 output s;
7 output cout;
8
9 wire half_sum, carry1, carry2;
10
11 assign half_sum = a ^ b;
12 assign carry1 = a & b;
13 assign carry2 = cin & half_sum;
14 assign s = half_sum ^ cin;
15 assign cout = carry1 | carry2;
```




Refer to sample code "adder\_1bit.v"

 

Credit:

<https://zh.m.wikipedia.org/zh-cn/File:Full-adder.svg>

# Module

   


Credit:

<https://zh.m.wikipedia.org/zh-cn/File:Full-adder.svg>

# Module

```
1 module adder_1bit(a, b, cin, s, cout);  
2  
3 input a, b;  
4 input cin;  
5  
6 output s;  
7 output cout;  
8  
9 wire half_sum, carry1, carry2;  
10  
11 assign half_sum = a ^ b;  
12 assign carry1 = a & b;  
13 assign carry2 = cin & half_sum;  
14 assign s = half_sum ^ cin;  
15 assign cout = carry1 | carry2;  
16  
17 endmodule
```

Refer to sample code "adder\_1bit.v"

 

# Data

- `<Width>'<Base><Value>`
- Width: width of bits
- Base: `b` for binary, `d` for decimal, `h` for hex
- e.g. `4'b1111 = 4'd15 = 4'hF`

# Combine 4 1-bit adders into a 4-bit adder


- Module instantiation
- Vector

# Module instantiation

- Instantiation predefined module
  - Not like function call, instantiation generates a real hardware component

```
adder_1bit bit0(a[0], b[0], cin, s[0], c0);  
adder_1bit bit1(a[1], b[1], c0, s[1], c1);  
adder_1bit bit2(a[2], b[2], c1, s[2], c2);  
adder_1bit bit3(a[3], b[3], c2, s[3], cout);
```

Refer to sample code "adder\_4bit.v"

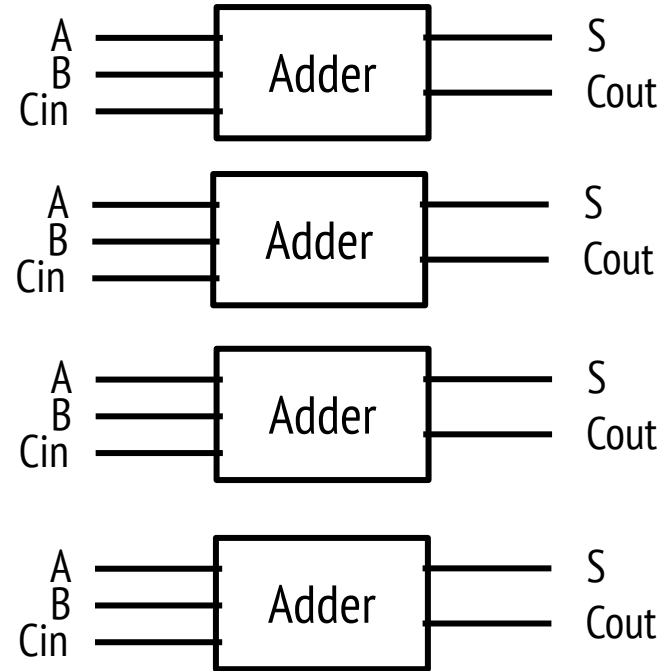


# Vector

- Wrap a set of wires into a vector
- Like an array of wires (Be careful of the notation)

```
input [3:0] a, b;
input cin;
output cout;
output [3:0] s;
```

Refer to sample code "adder\_4bit.v"

 




# Put them all together

```
1 module adder_4bit(a, b, cin, s, cout);  
2  
3   input [3:0] a, b;  
4   input cin;  
5   output cout;  
6   output [3:0] s;  
7  
8   wire c0, c1, c2;  
9  
10  adder_1bit bit0(a[0], b[0], cin, s[0], c0);  
11  adder_1bit bit1(a[1], b[1], c0, s[1], c1);  
12  adder_1bit bit2(a[2], b[2], c1, s[2], c2);  
13  adder_1bit bit3(a[3], b[3], c2, s[3], cout);  
14  
15 endmodule
```

Refer to sample code "adder\_4bit.v"


naive ripple carry (slow)

 

# Sequential logic
 
## Next, let's build an accumulator

- 4 bit adder as combinational part
- 4 bit register to save the state




# Register

- Use **reg** to declare a register

```
reg [3:0] register;
```

Refer to sample code "register\_4bit.v"

 


# Clock

- Use an always block to sense the clock signal that the registers is using

```
6  reg [3:0] register;
7
8  assign out = register;
9  always @(posedge clk) begin
10     register = in;
11 end
```


Refer to sample code "register\_4bit.v"

 

# Combine the components

```
1 module accumulator(clk, out);  
2   input clk;  
3   output [3:0] out;  
4   reg [3:0] register;  
5   wire [4:0] added;  
6  
7   adder_4bit adder(register, 4'b1, 1'b0, added[3:0], added[4]);  
8  
9   always @(posedge clk) begin  
10    out = added[3:0];  
11  end  
12 endmodule
```

Refer to sample code ".accumulator.v"

 


# Combine the components

The code doesn't work. Why?

```
1 module accumulator(clk, out);  
2   input clk;  
3   output [3:0] out;  
4   reg [3:0] register;  
5   wire [4:0] added;  
6  
7   adder_4bit adder(register, 4'b1, 1'b0, added[3:0], added[4]);  
8  
9   always @(posedge clk) begin  
10    out = added[3:0];  
11  end  
12 endmodule
```

Refer to sample code ".accumulator.v"

 


# What is the state in the beginning?

```
1 module accumulator(clk, out);  
2   · input clk;  
3   · output [3:0] out;  
4   · reg [3:0] register;  
5   · wire [4:0] added;  
6  
7   · adder_4bit adder(register, 4'b1, 1'b0, added[3:0], added[4]);  
8  
9   · always @(posedge clk) begin  
10    · out = added[3:0];  
11  · end  
12 endmodule
```

Refer to sample code ".accumulator.v"

Initial Problem: reg = 4b'xxxx

 


JAKE-CLARK.TUMBLR



 
# Add a reset signal for initializing

- Reset all register to 0 if reset in 0
- Do what accumulator do otherwise


 
# Add a reset signal for initializing

- Reset all register to 0 if reset in 0
- Do what accumulator do otherwise
- To achieve this, we need a multiplexer




# Multiplexer

- Use **if** statement in always block

```
8  always @(*) begin
9    if (sel)
10     out = a;
11  else
12     out = b;
13  end
```

Refer to sample code "multiplexer.v"

 


# Multiplexer

- Use `? :`

```
3 input a, b, sel;
4 output out;
5
6 assign out = sel ? a : b;
```


Refer to sample code "multiplexer.v"

 

# Add a reset signal for initializing

```
1 module accumulator(rst, clk, out);  
2   input rst;  
3   input clk;  
4   output [3:0] out;  
5   reg [3:0] register;  
6   wire [4:0] added;  
7  
8   assign out = register;  
9   adder_4bit adder(register, 4'b0001, 1'b0, added[3:0], added[4]);  
10  
11   always @(posedge clk or negedge rst) begin  
12     if (rst)  
13       register = added[3:0];  
14     else  
15       register = 4'b0;  
16   end  
17 endmodule
```

Refer to sample code "accumulator.v"

 


# Testbench

# Testbench

- To test your verilog module
- There is something that is non-synthesizable
  - e.g. timing, variable dump...

# How can we test a module?

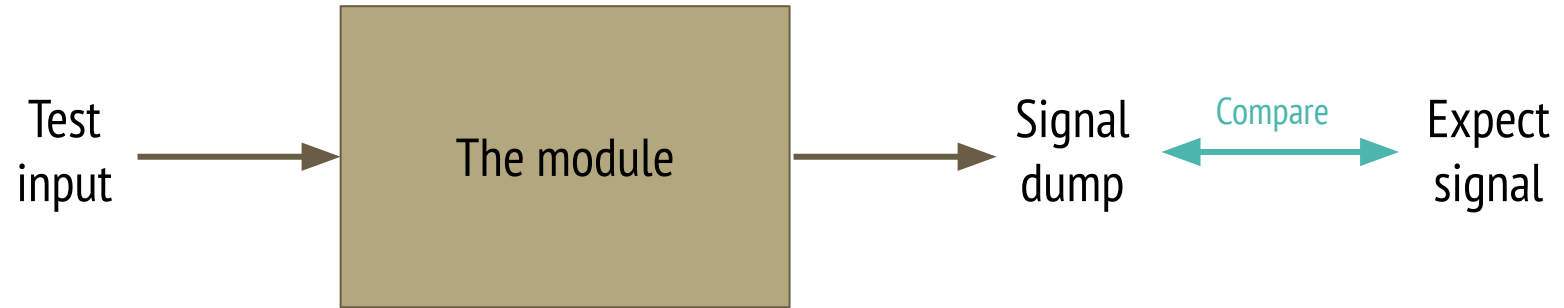



# Testbench workflow

1. Initialize the testing environment
2. Send the test inputs
3. Finish the test

# Testbench workflow


1. Initialize the testing environment
2. Send the test inputs
3. Finish the test

```
1  module sample_test;↵
2  ↵
3  reg signal;↵
4  ↵
5  initial begin↵
6  ..// dump signal into "sample_test.vcd"↵
7  ..$dumpfile("sample_test.vcd");↵
8  ..// dump all signals↵
9  ..$dumpvars;↵
10 ..signal = 1'b1;↵
11 ..#10↵
12 ..signal = 1'b0;↵
13 ..#15↵
14 ..signal = 1'b1;↵
15 ..#100↵
16 ..$finish;↵
17 end↵
18 ↵
19 endmodule↵
```

Refer to sample code "sample\_test.v"
 
# Testbench workflow


```
1 module sample_test;
2
3 reg signal;
4
5 initial begin
6   // dump signal into "sample_test.vcd"
7   $dumpfile("sample_test.vcd");
8   // dump all signals
9   $dumpvars;
10  signal = 1'b1;
11  #10
12  signal = 1'b0;
13  #15
14  signal = 1'b1;
15  #100
16  $finish;
17 end
18
19 endmodule
```



 
# Testbench workflow

- Use always block for periodic signal

```
1 module sample_test;
2
3 reg signal;
4 reg periodic;
5
6 initial begin
7   // dump signal into "sample_test.vcd"
8   $dumpfile("sample_test.vcd");
9   // dump all signals
10  $dumpvars;
11  signal = 1'b1;
12  periodic = 1'b0;
13  #10
14  signal = 1'b0;
15  #15
16  signal = 1'b1;
17  #100
18  $finish;
19 end
20
21 always #10 periodic = ~periodic;
22
23 endmodule
```



# Testbench of accumulator

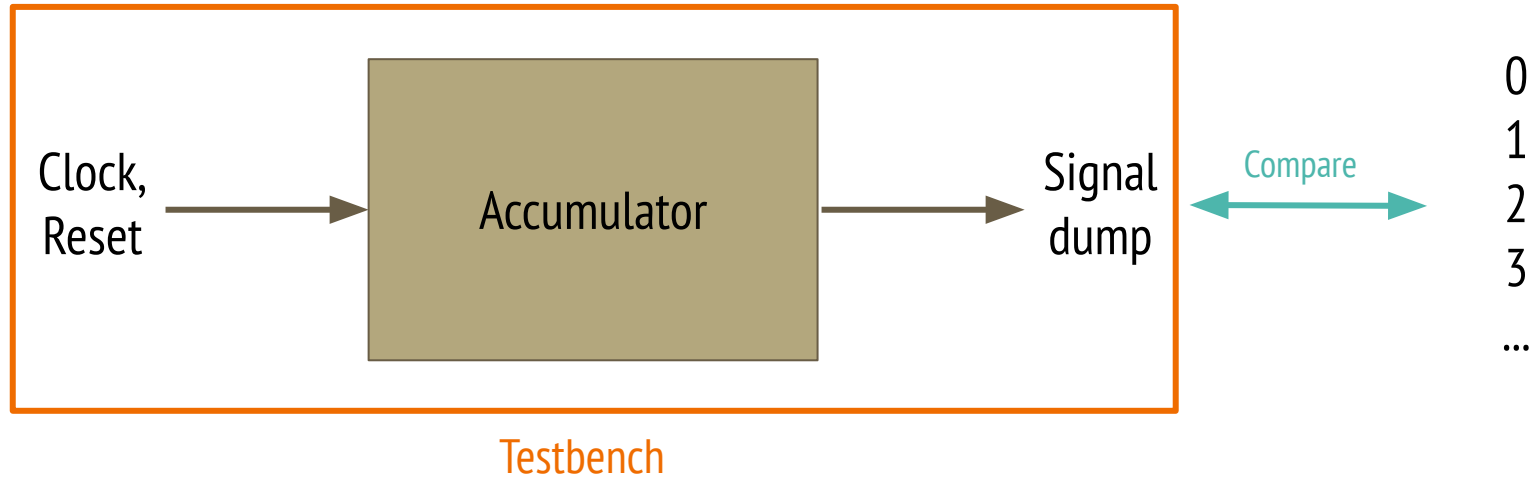

# Testbench workflow

1. Reset accumulator by **reset signal**
2. Generate an **1hz clock** signal
3. Display the value of the accumulator every cycle
4. Finish the test after 30 sec

# Testbench workflow

1. Reset accumulator by **reset** signal
2. Generate an **1hz** **clock** signal
3. Display the value of the accumulator every cycle
4. Finish the test after 30 sec

```
1 module test;
2
3 reg reset, clock;
4 wire [3:0] out;
5
6 accumulator acc(reset, clock, out);
7
8 initial begin
9     $dumpfile("test.vcd");
10    $dumpvars;
11
12    clock = 1'b0;
13    reset = 1'b0;
14
15    #0.1
16    reset = 1'b1;
17
18    #30
19    $finish;
20 end
21
22 always #0.5 begin
23     clock = ~clock;
24     if (clock)
25         $display("%d", out);
26 end
27
28 endmodule
```

# Testbench output

```
(base) jup@jup-Inspiron-14-5425:~/projecting/verilog_tutorial$ vvp test
VCD info: dumpfile test.vcd opened for output.
0
1
2
3
4
5
6
7
8
9
10
11
12
13
14
```



# Wave



# Tool usage

# iverilog

- iverilog [-o output\_name] source-file(s)
- e.g. iverilog -o test source1.v source2.v

# vvp

- vvp file\_name


# GTKwave

- gtkwave filename

# GTKwave

Modules

Signals of the module

 

wave