



# Verilog lab



# HDLBits

- [https://hdlbits.01xz.net/wiki/Problem\\_sets](https://hdlbits.01xz.net/wiki/Problem_sets)

# Wire & vector

1. Four wires
2. Vectors
3. Vectors in more detail
4. Vector part select

# Logic gate

1. Inverter
2. AND gate
3. Declaring wires

# Combinational logic

1. [Simple circuit A](#)
2. [Thermostat](#)

# Module

1. Adder 1
2. Adder-subtractor

# Sequential logic

1. Always blocks (clocked)
2. Four-bit binary counter

# Testbench



1. Clock
2. Testbench1



# Accumulator


input: reset, clock

output: value of the accumulator

  
 
# Baby ALU

- A simple 8 bit ALU
- Instruction
  - AND (ALUop 2'b00)
  - ADD (ALUop 2'b00)
  - SUB (ALUop 2'b00)
  - SRAI (ALUop 2'b00)



# Baby ALU

- A simple 8 bit ALU
- Instruction
  - AND (ALUop 2'b00)
  - ADD (ALUop 2'b00)
  - SUB (ALUop 2'b00)
  - SRAI (ALUop 2'b00)

