
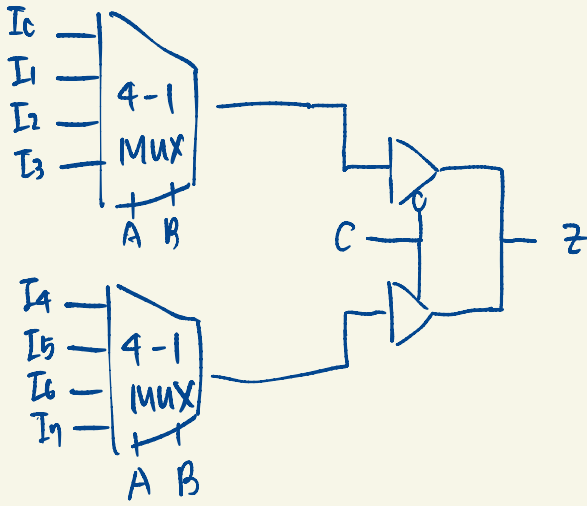


1.

 

2.

$A$	$B$	$Q$	$Q^+$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



$\therefore$  output of OR gate  $Q = R + p'$

$$\Rightarrow \underline{Q} = R + p' \stackrel{\substack{\uparrow \\ \therefore p = Q'}}{=} R + (Q)' = \underline{R + Q}$$

$$\Rightarrow R = 0 \dots \textcircled{1}$$

$\therefore$  output of AND gate  $p' = Q \cdot H$

$$\therefore Q = R + p' \Rightarrow p' = (R + p')H$$

$$\Rightarrow Q = (R + Q)H = \overset{0}{R}H + QH = QH$$

$$\therefore Q = QH \Rightarrow H = 1 \dots \textcircled{2}$$

$$\therefore \textcircled{1} \text{ \& } \textcircled{2} \Rightarrow R = 0, H = 1$$

(b).

R	H	Q	$Q^+$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	X
1	0	1	X
1	1	0	1
1	1	1	1


when  $R=1$  &  $H=0$ :  $\begin{cases} Q=1 \\ p'=0 \Rightarrow p=1 \end{cases}$   
 $\therefore p = Q' \Rightarrow$  not allowed.

Q \ RH	00	01	11	10
0	0	0	1	not allowed
1	0	1	1	not allowed


$$\Rightarrow Q^+ = RH + QH$$

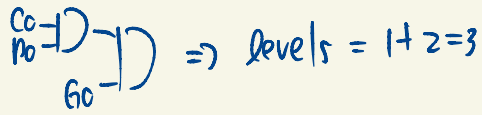7.


1 bit:  $\begin{matrix} A \\ B \end{matrix} \rightarrow \text{AND} - G +$   
 $\begin{matrix} A \\ B \end{matrix} \rightarrow \text{AND} - P$



2 bit:  $-11-+$

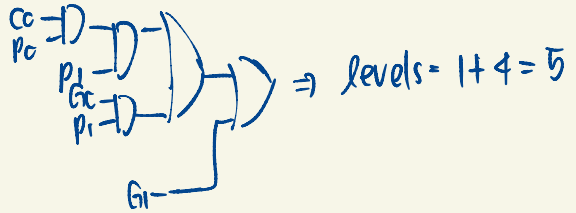

3 bit:  $-11-+$

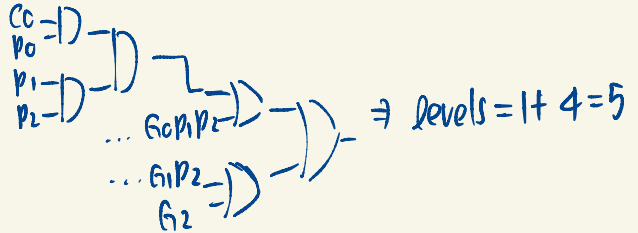

$\Rightarrow \# \text{ of levels } F(n) = \underset{\substack{\uparrow \\ \text{for prod}}}{1} + \underset{\substack{\uparrow \\ \text{and xor gate}}}{2} \cdot (\lceil \log_2(n+1) \rceil)$

File Edit Search Time Markers View Help

 From: 0 sec To: 3276800 ns  Marker: 3100300 ps | Cursor: 2870600 ps


SST

- lab1\_main
  - adder
    - testcla
      - c\_op\_0p\_1
      - c\_op\_0p\_1p\_2
        - c\_1
        - c\_2
        - c\_3
        - fa\_0
        - fa\_1
        - fa\_2
        - g\_0
          - g\_0p\_1
          - g\_0p\_1p\_2
            - g\_1
            - g\_1p\_2
            - g\_2
            - p\_0

Signals

Time  
A[2:0] = 000  
B[2:0] = 111  
C0 = 1  
S[2:0] = 000

Waves

 

Type	Signals
------	---------

wire	A[2:0]
wire	B[2:0]
wire	C0
wire	C1
wire	C2
wire	C3
wire	S[2:0]
wire	c0p0p1
wire	c0p0p1p2
wire	g0p1
wire	g0p1p2
wire	g1p2
wire	g[2:0]
wire	p[2:0]
wire	pc0
wire	temp0
wire	temp1
wire	temp2

Filter:

Append	Insert	Replace
--------	--------	---------

4.

(1).

```
module rca_gl(  
    output C3,          // carry output  
    output[2:0] S,      // sum  
    input[2:0] A, B,    // operands  
    input C0            // carry input  
);  
  
    // TODO:: Implement gate-level RCA  
    FA fa_0(C1, S[0], A[0], B[0], C0);  
    FA fa_1(C2, S[1], A[1], B[1], C1);  
    FA fa_2(C3, S[2], A[2], B[2], C2);  
endmodule
```

(2).

```
module cla_gl(  
    output C3,          // carry output  
    output[2:0] S,      // sum  
    input[2:0] A, B,    // operands  
    input C0            // carry input  
);  
  
    // TODO:: Implement gate-level CLA  
    wire [2:0] p, g;  
    //0: first bit  
    AND g_0(g[0], A[0], B[0]);  
    OR p_0(p[0], A[0], B[0]);  
    AND pc_0(pc0, p[0], C0);  
    OR c_1(C1, g[0], pc0);  
    FA fa_0(temp0, S[0], A[0], B[0], C0);  
  
    //1: second bit  
    AND g_1(g[1], A[1], B[1]);  
    OR p_1(p[1], A[1], B[1]);  
    AND4 c_0p_0p_1(c0p0p1, C0, p[0], p[1], 1'b1);  
    AND g_0p_1(g0p1, g[0], p[1]);  
    OR4 c_2(C2, g[1], g0p1, c0p0p1, 1'b0);  
    FA fa_1(temp1, S[1], A[1], B[1], C1);  
  
    //2: third bit  
    AND g_2(g[2], A[2], B[2]);
```

```

    OR p_2(p[2], A[2], B[2]);
    AND4 c_0p_0p_1p_2(c0p0p1p2, C0, p[0], p[1], p[2]);
    AND4 g_0p_1p_2(g0p1p2, g[0], p[1], p[2], 1'b1);
    AND g_1p_2(g1p2, g[1], p[2]);
    OR4 c_3(C3, g[2], g1p2, g0p1p2, c0p0p1p2);
    FA fa_2(temp2, S[2], A[2], B[2], C2);

endmodule

```

## 6. (a) Maximum propagation delay for rca\_gl (ripple carry adder)

```

justin@DESKTOP-DSHM2G6:/mnt/c/Users/justi/OneDrive/Desktop/LAB-01$ iverilog -o lab1_compiled.vvp lab1.v
justin@DESKTOP-DSHM2G6:/mnt/c/Users/justi/OneDrive/Desktop/LAB-01$ vvp lab1_compiled.vvp
VCD info: dumpfile lab1.vcd opened for output.
The maximum delay is 23 ticks on transition 000+000+0 --> 000+111+1
justin@DESKTOP-DSHM2G6:/mnt/c/Users/justi/OneDrive/Desktop/LAB-01$

```

## (b) Maximum propagation delay for cla\_gl (carry lookahead adder)

```

justin@DESKTOP-DSHM2G6:/mnt/c/Users/justi/OneDrive/Desktop/LAB-01$ iverilog -o lab1_compiled.vvp lab1.v
justin@DESKTOP-DSHM2G6:/mnt/c/Users/justi/OneDrive/Desktop/LAB-01$ vvp lab1_compiled.vvp
VCD info: dumpfile lab1.vcd opened for output.
The maximum delay is 20 ticks on transition 000+000+0 --> 000+011+1
justin@DESKTOP-DSHM2G6:/mnt/c/Users/justi/OneDrive/Desktop/LAB-01$ _

```